

# P2 Digital Electronics

## Lecture 5: Integration of digital logic components: Multiplexers, ROMs and PLAs

Mark Cannon

[mark.cannon@eng.ox.ac.uk](mailto:mark.cannon@eng.ox.ac.uk)

Trinity Term 2026



# Overview of lectures

1. Logical functions and logic gates
2. Low level logic design
3. Binary number representation
4. Binary arithmetic
- 5. Integration of digital logic components**
6. Memory and sequential circuits
7. Design of sequential logic
8. Data converters: analogue to digital / digital to analogue

Please send feedback, comments and corrections to [mark.cannon@eng.ox.ac.uk](mailto:mark.cannon@eng.ox.ac.uk)
  
# From transistor to large scale integration



- ▶ Transistor
- ▶ Logic Gate
- ▶ SSI – Small Scale Integration chips with a few 10s of transistors
- ▶ MSI – Medium Scale Integration chips with  $\sim 100$  of transistors
- ▶ LSI – Large Scale Integration chips with  $\sim 10^4$  transistors
- ▶ VLSI/ULSI - Very Large Scale Integration chips with  $\sim 10^9$  transistors


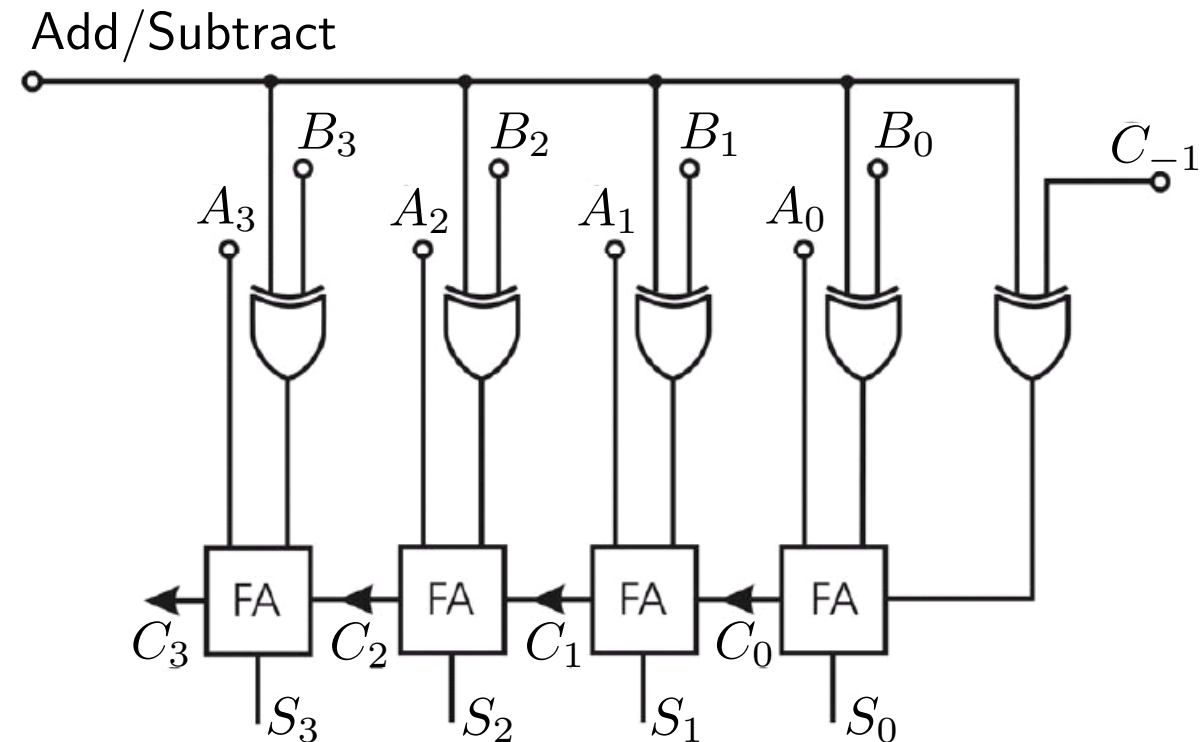 
# Arithmetic Logic Unit

The part of a CPU that does numerical calculations

- ▶ Contains a full ripple adder (8-bit, 16-bit etc)
- ▶ Driven by control lines ( $\pm$ )
- ▶ Two input numbers
- ▶ One output
- ▶ Flags indicate fault conditions
  - ★ Carry-out
  - ★ Overflow
  - ★ Underflow






# Outline of lecture 5

- ▶ Electronic integration
- ▶ Multiplexers (MUX)
- ▶ Bus and tri-state connections
- ▶ Read only Memory (ROM)
  - ▷ Decoder
  - ▷ Use of ROMs
- ▶ Programmable logic array (PLA)

# Multiplexers

 


A multiplexer is a digital switch


It selects which data stream or bit is sent to the next section of a circuit

Can be used to perform simple logic programming


# MUX logic

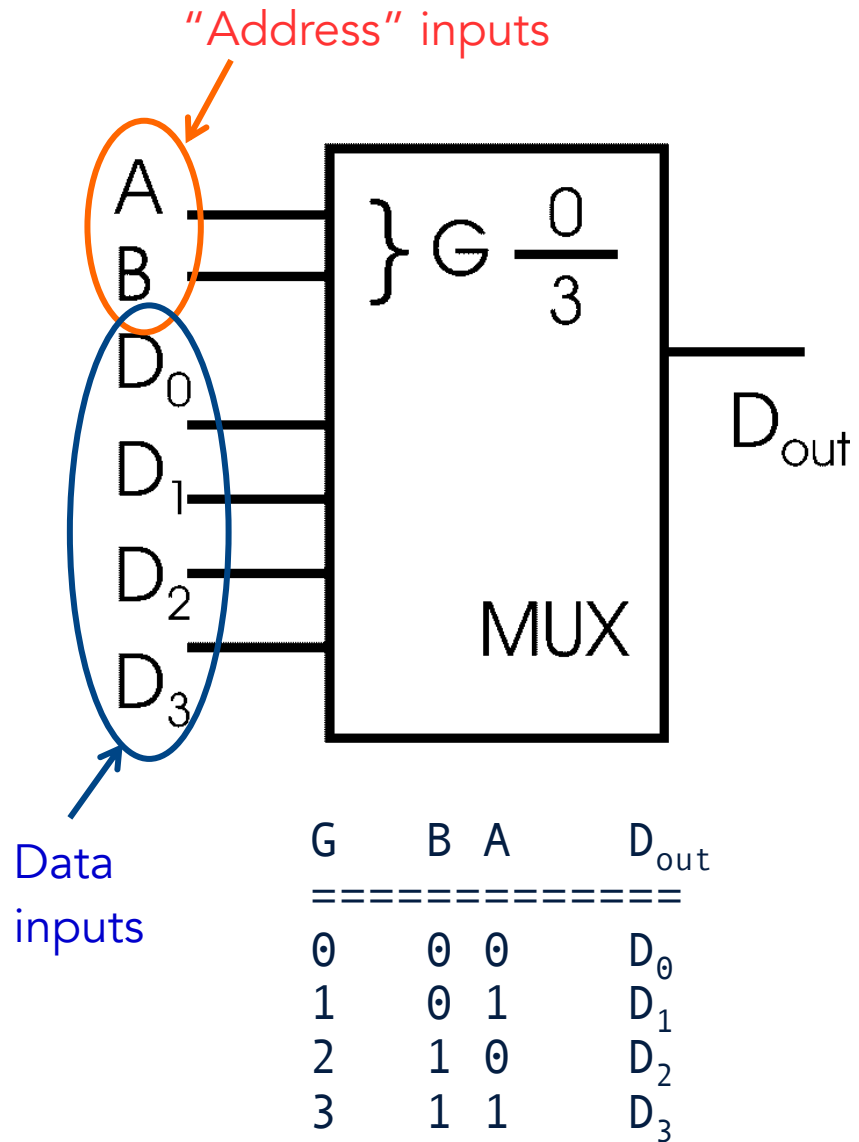

 
$$D_{out} = \bar{A}.\bar{B}.D_0 + A.\bar{B}.D_1 + \bar{A}.B.D_2 + A.B.D_3$$



# Buses and tri-state outputs

 

 
Integrated circuits often have a very large number of inputs and outputs.



Many digital lines uses up a lot of printed circuit board space.




 Parallel data lines called **buses** are used to transport digital data around a system



Not very scalable,  
modern architectures are  
64 bits!  
Multiple peripherals are  
connected to the CPU

# Bus architecture

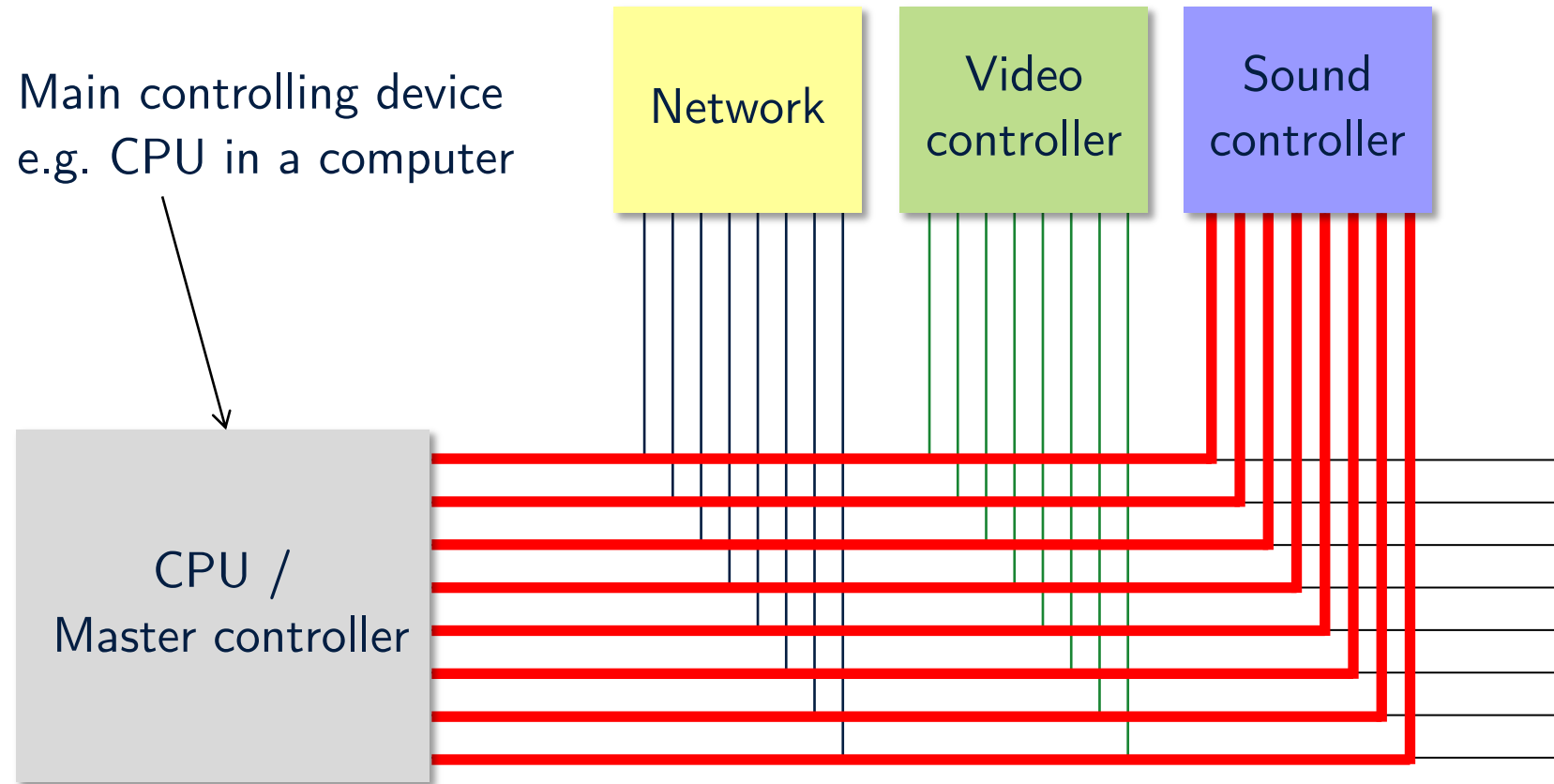


Bus lines (wires) shared between all peripherals  
as many as 64 or more in many cases


# Bus conflicts

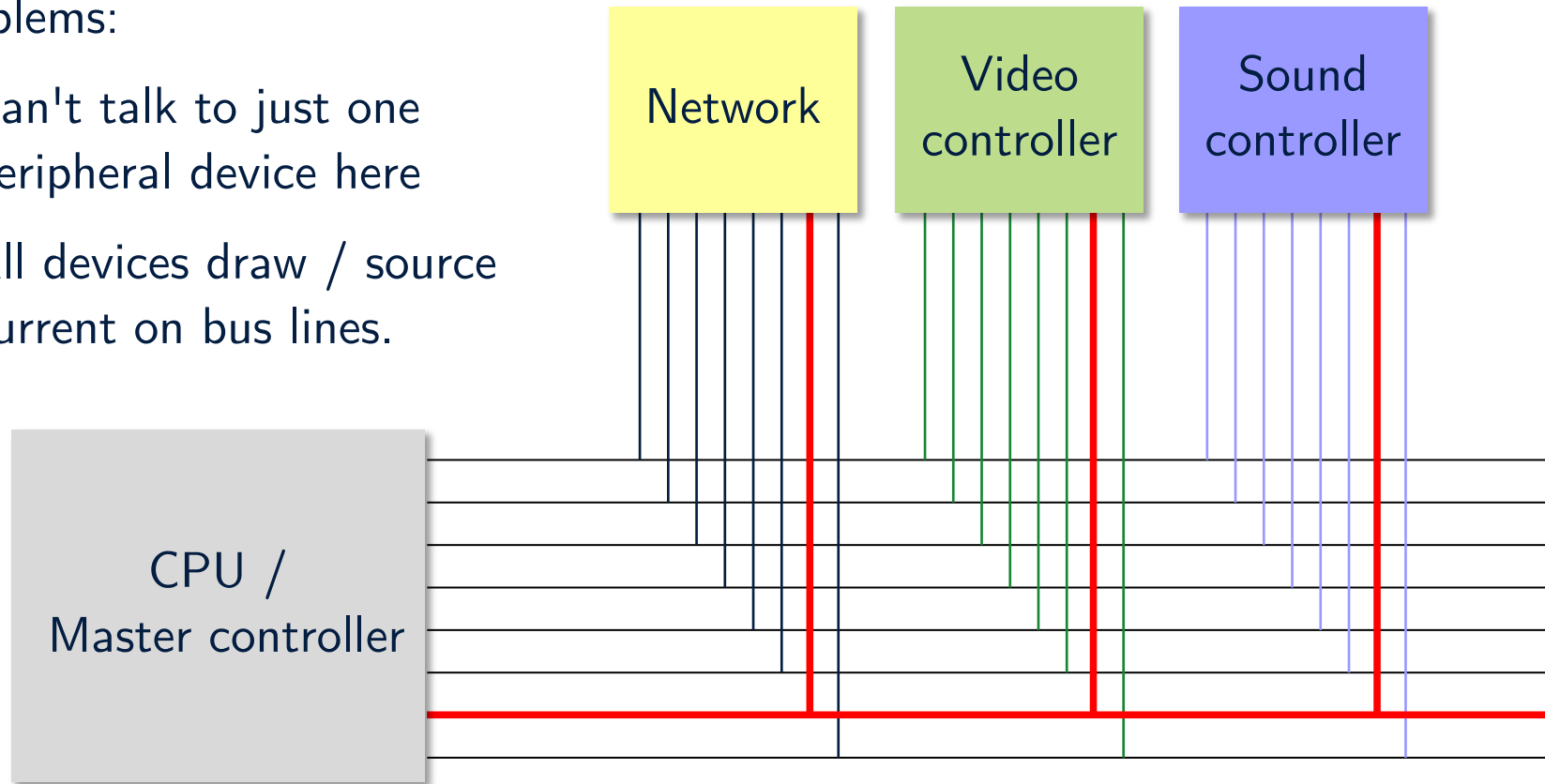Problems:

- Can't talk to just one peripheral device here
- All devices draw / source current on bus lines.



# Bus conflicts

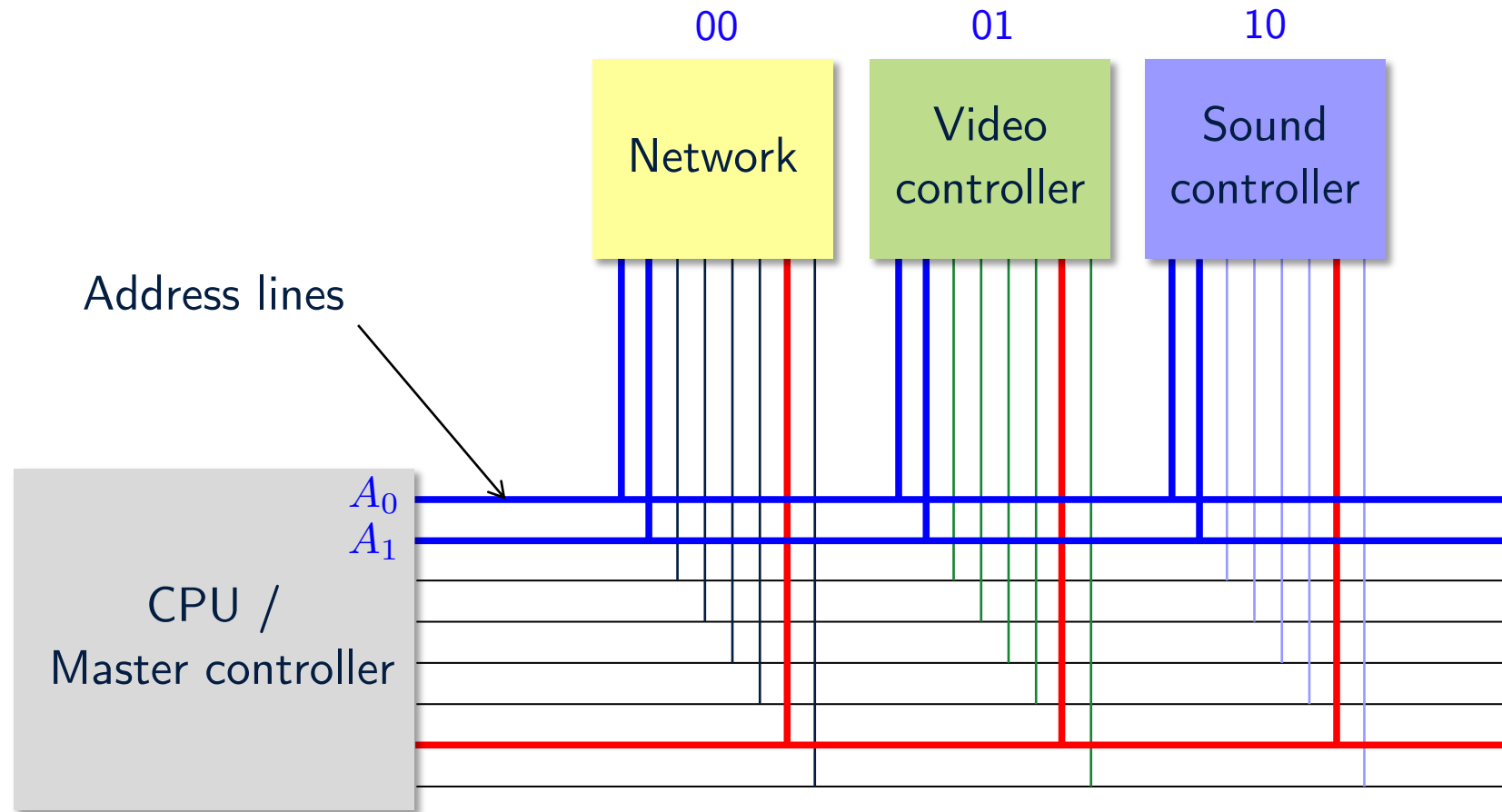

Problem: Although we can now select which peripheral to talk to, the others are still connected and can draw current from bus lines and confuse data levels...

Solution: ensure unwanted peripherals 'disconnect' from bus lines


# Tri-state outputs

Add an extra logic state to outputs:


- ★ High (1)
- ★ Low (0)
- ★ High impedance (draws no current)



 Allows outputs to become isolated from bus lines



Tri state symbol

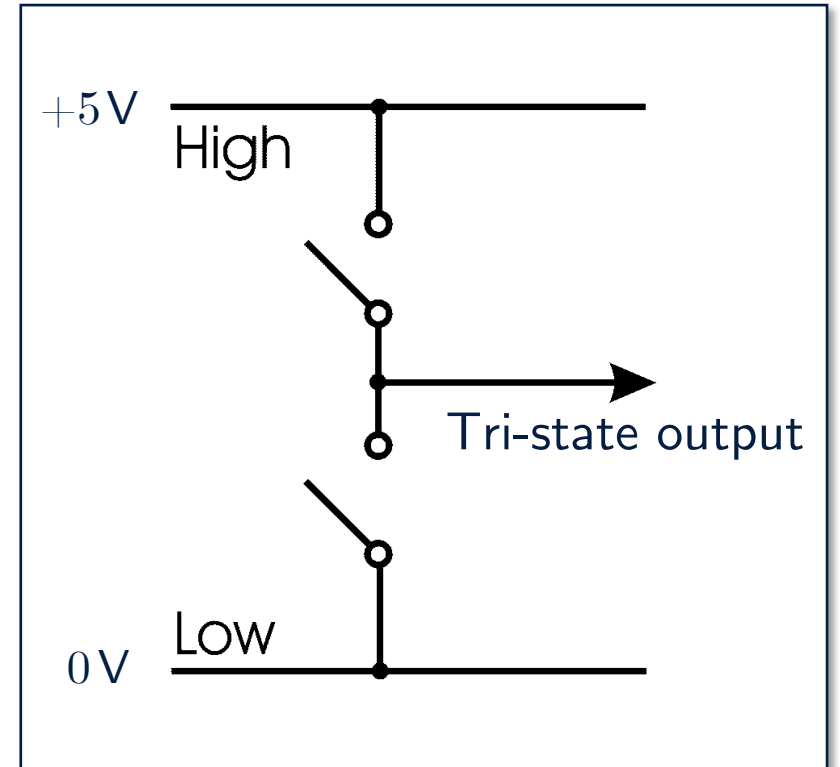



# Chip select and output enable

Chip select – switches on chip inputs

- ★ makes ROM read input address  $A_7 \dots A_0$
- ★ address lines draw no power when disabled

Output enable – connects outputs

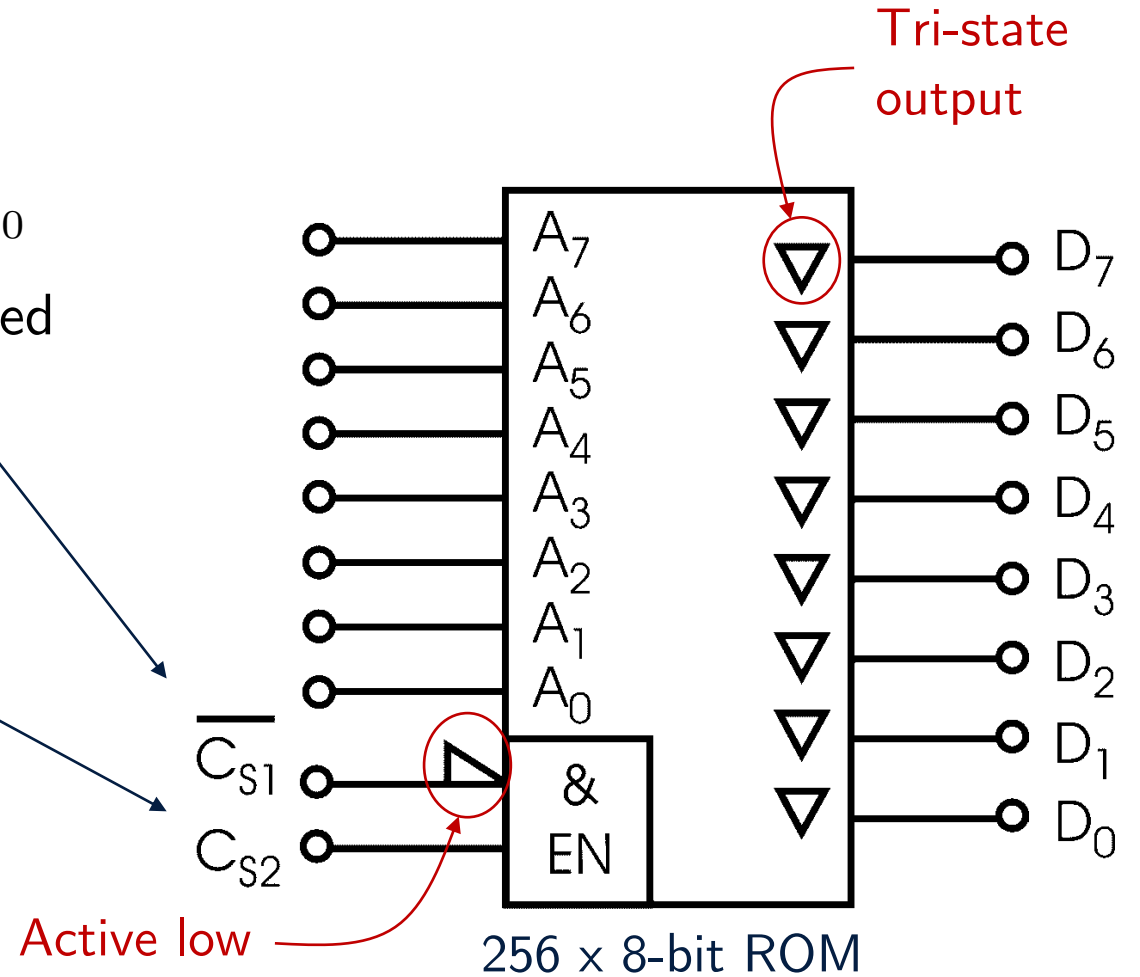 
- ★ allows data output from  $D_7 \dots D_0$
- ★ data lines draw no power when disabled


 
# ROM – read only memory

ROM = look-up table

- ★ Table contents fixed by design
- ★ Can implement any truth table, but relatively inefficient for implementing logic functions



3-bit wide address space with 5-bit wide data

# How a ROM works


- ▷  $n \times m$  ROM:  $n$  address bits,  $m$  data bits
- ▷ Decoder: converts input binary number to drive one of  $2^n$  control lines
- ▷  $2^n \times m$  matrix of digital switches to store bits of data
- ▷ Output stage to OR the outputs from each of the  $m$  columns

**AND**

a	b	a.b
0	0	0
0	1	0
1	0	0
1	1	1

**OR**

a	b	a+b
0	0	0
0	1	1
1	0	1
1	1	x

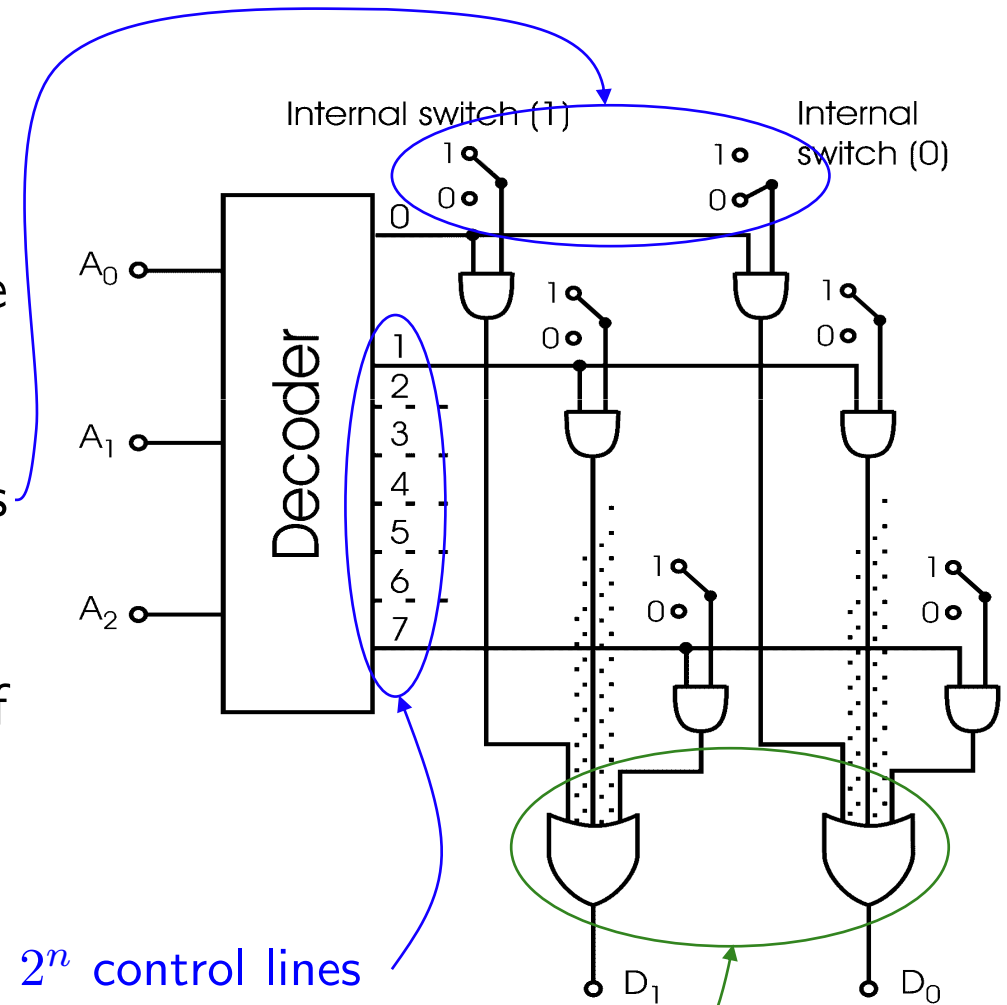


$2^n$  control lines

Output:  $2^n$ -input OR gates


# Decoder truth table

$A_2$	$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

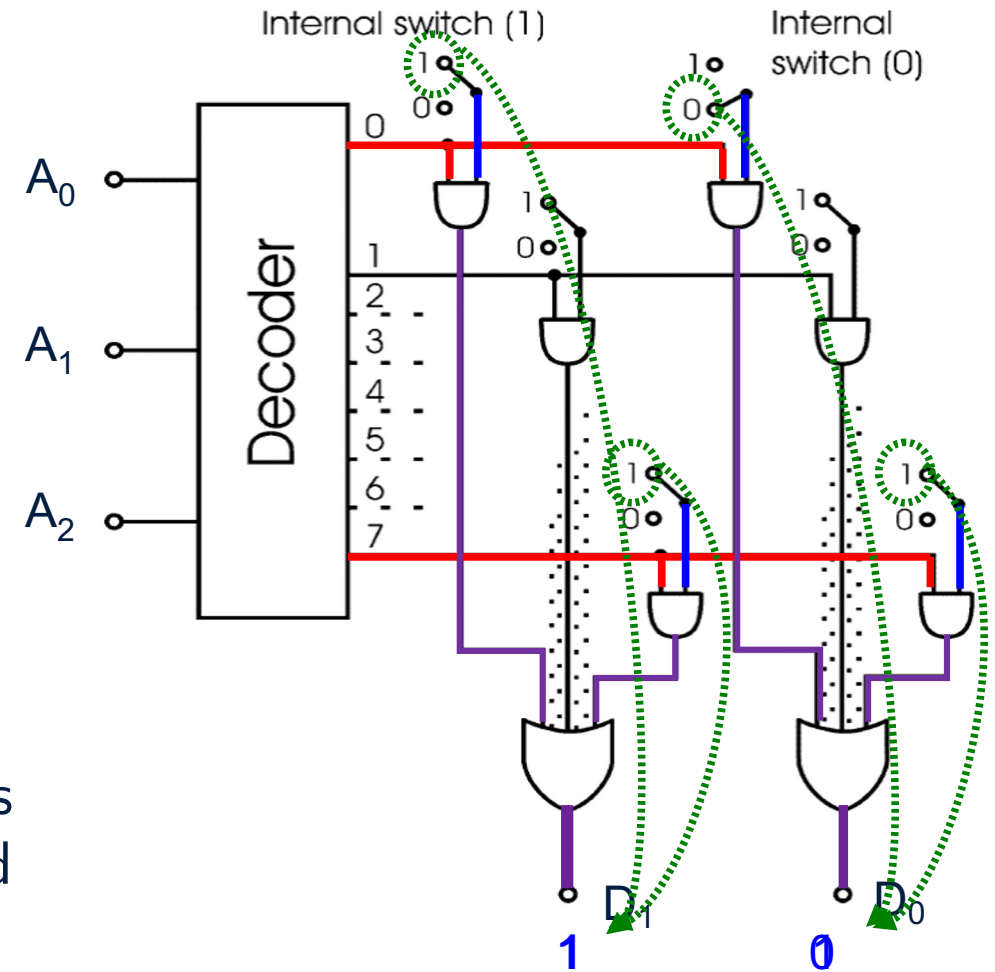
The Decoder ensures that only one control line is activated at any time instant, so only the selected stored data is connected to the output



# The decoder

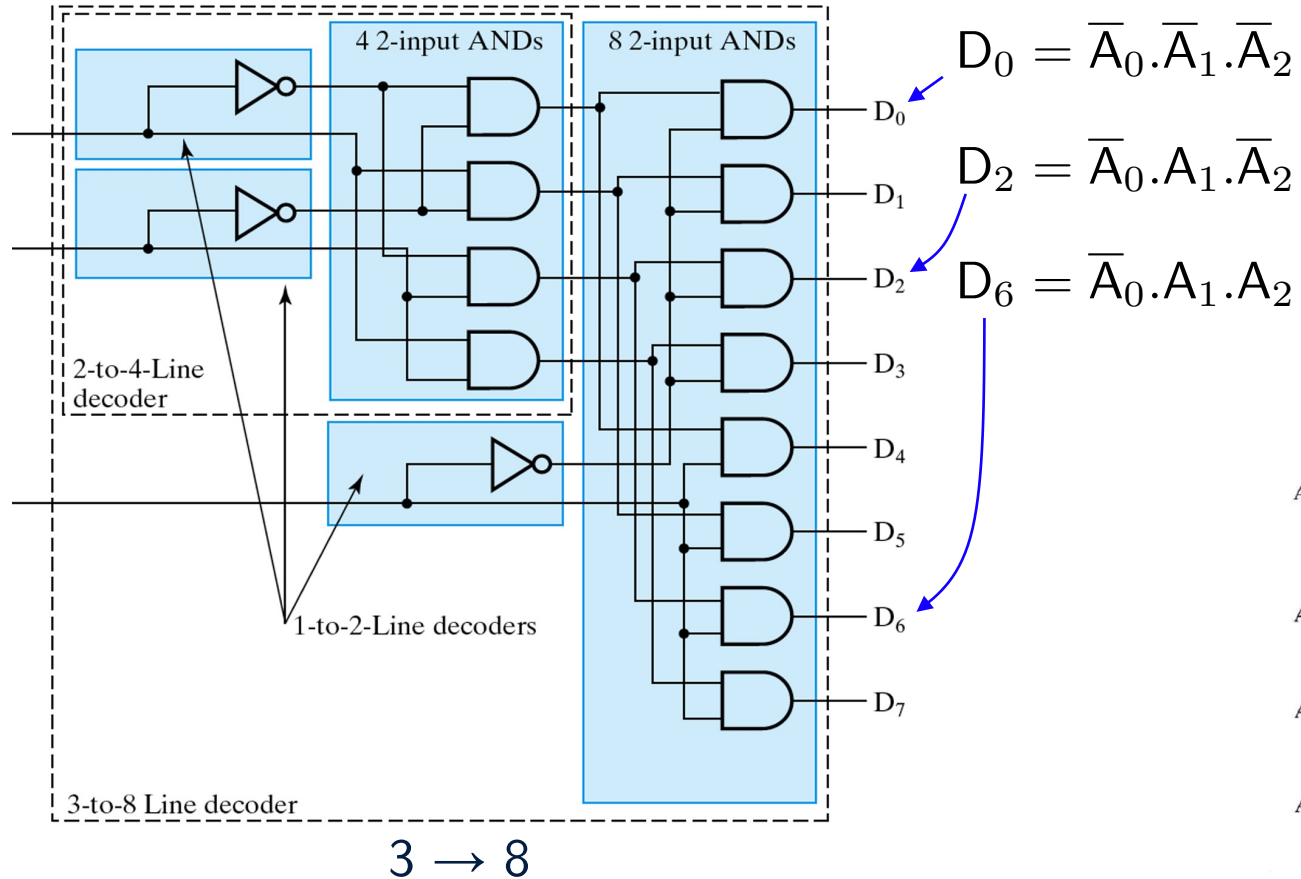


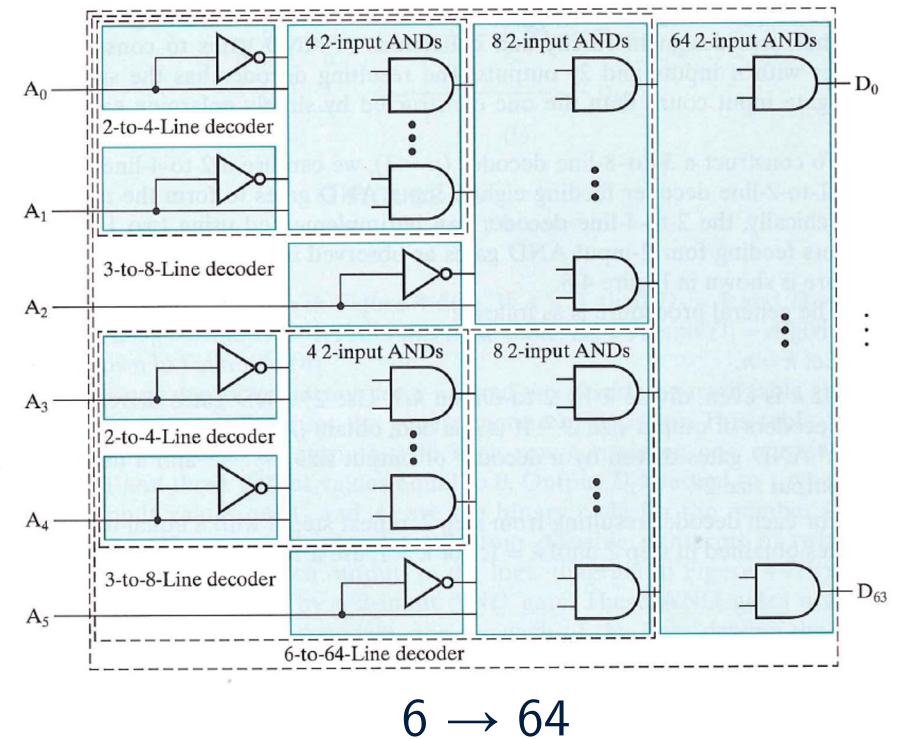- ★ Similar in form to the multiplexer
- ★ Can become very complex when there are lots of address bits



 
# ROM usage

- ▶ **ROM** is 'non-volatile' memory so doesn't disappear when power is switched off; data is written by manufacturer
- ▶ **PROM** (Programmable ROM) is non-volatile, but can be programmed once using a special device
- ▶ Use a ROM (or PROM) to implement a required truth table
- ▶ **EPROMs** and **EEPROMs** can be erased and re-programmed multiple times. EPROM is erasable by UV light, EEPROM by electricity





4 Mbit EPROM

 

EEPROM inside a SIM card


# Code converter: 7 segment display

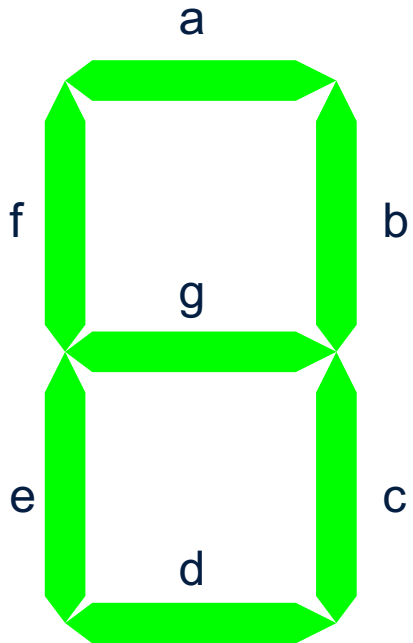 



$x_3$	$x_2$	$x_1$	$x_0$	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	0	1	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
 
# outputs


- 
- 0 abcdef
  - 1 bc
  - 2 abdeg
  - 3 abcdg
  - 4 bcfg
  - 5 acdfg
  - 6 bcdefg
  - 7 abc
  - 8 abcdefg
  - 9 abcdfg



# Code converter: 7 segment display

  


$x_3$	$x_2$	$x_1$	$x_0$	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1

 

$$a = x_1 + x_3 \cdot x_2 + \overline{x_0} \cdot x_3 + \overline{x_2 \oplus x_0}$$
 
# outputs


- 
- 0 abcdef
  - 1 bc
  - 2 abdeg
  - 3 abcdg
  - 4 bcfg
  - 5 acdfg
  - 6 bcdefg
  - 7 abc
  - 8 abcdefg
  - 9 abcdfg



# What is a logic gate?


- A circuit constructed from transistors that implements a logic expression?
- Or any device that implements a logic expression?
- Mechanical gates: <https://www.youtube.com/watch?v=HGNSLtT2wXw>, [https://www.youtube.com/watch?v=5X\\_Ft4YR\\_wU](https://www.youtube.com/watch?v=5X_Ft4YR_wU), <https://www.randomwraith.com/logic.html>

- Fluidic logic gates

 

<https://www.youtube.com/watch?v=T3-3Y8gDbPA>

## DNA logic gates

 


J. Am. Chem. Soc., 2004, 126 (30), pp 9458-9463

# Programmable Logic Array (PLA)


A PLA is a chip capable of implementing any sum-of-products logic function

- ▶ Contains OR and AND gates and logic to link them together
- ▶ During programming, permanent links are made between inputs and outputs
- ▶ More efficient than ROM for simple logic functions
- ▶ Generally, can only program once using a special programmer
- ▶ Precursors to modern, more sophisticated field programmable gate arrays (FPGAs)


# Programmable Logic Array (PLA)

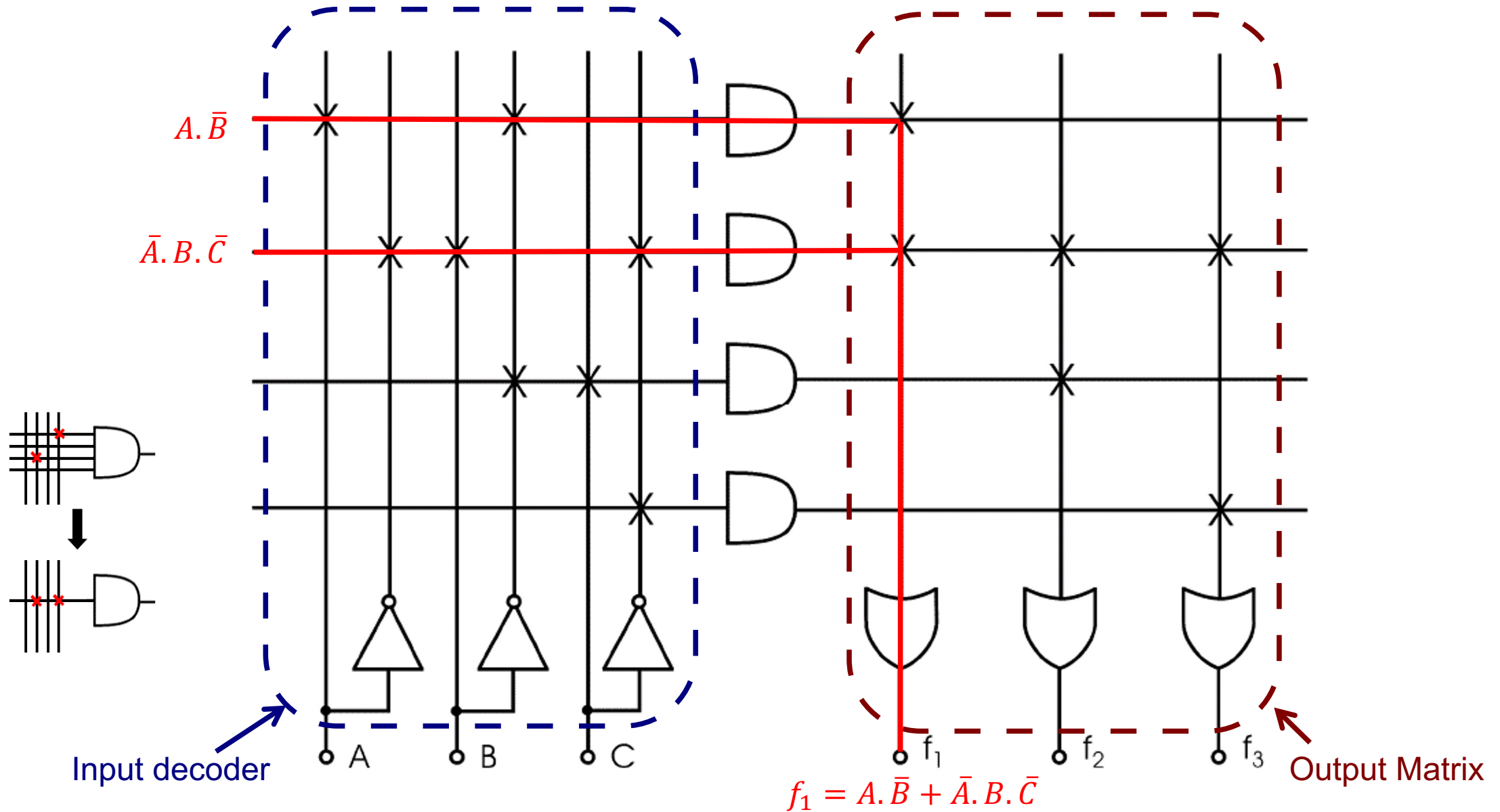

# Creating a memory: a simple latch

 


A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

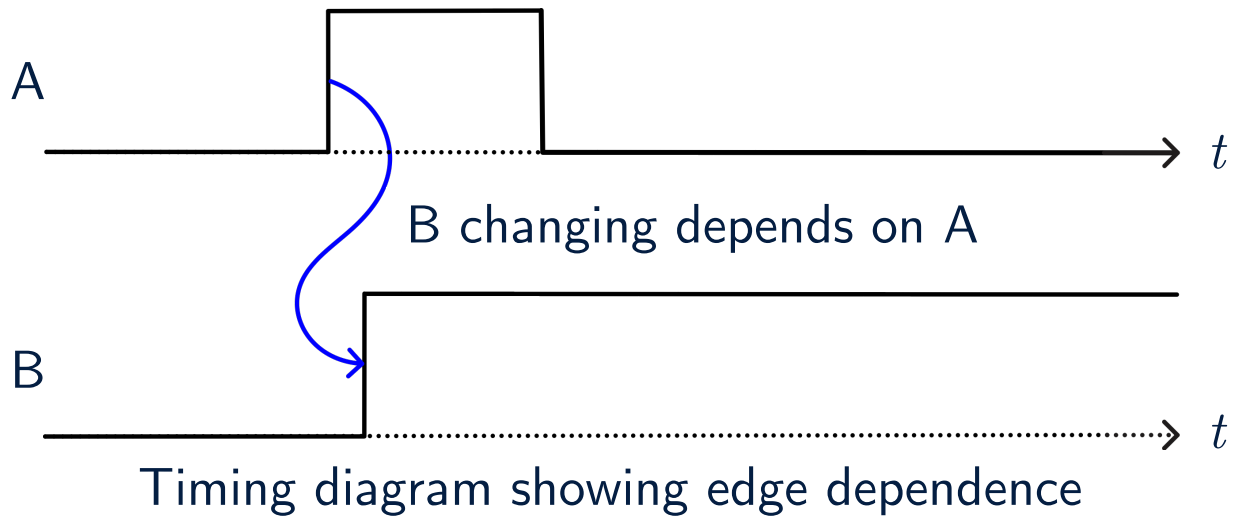

The feedback allows us to record an event (A changing from 0 to 1) ... but we can't set B back to 0!


 
# Including a reset

We need a way to make the feedback signal go to 0 when we want to store a 0 bit



Next value of output:  $B_{n+1} = B_n + A$

 
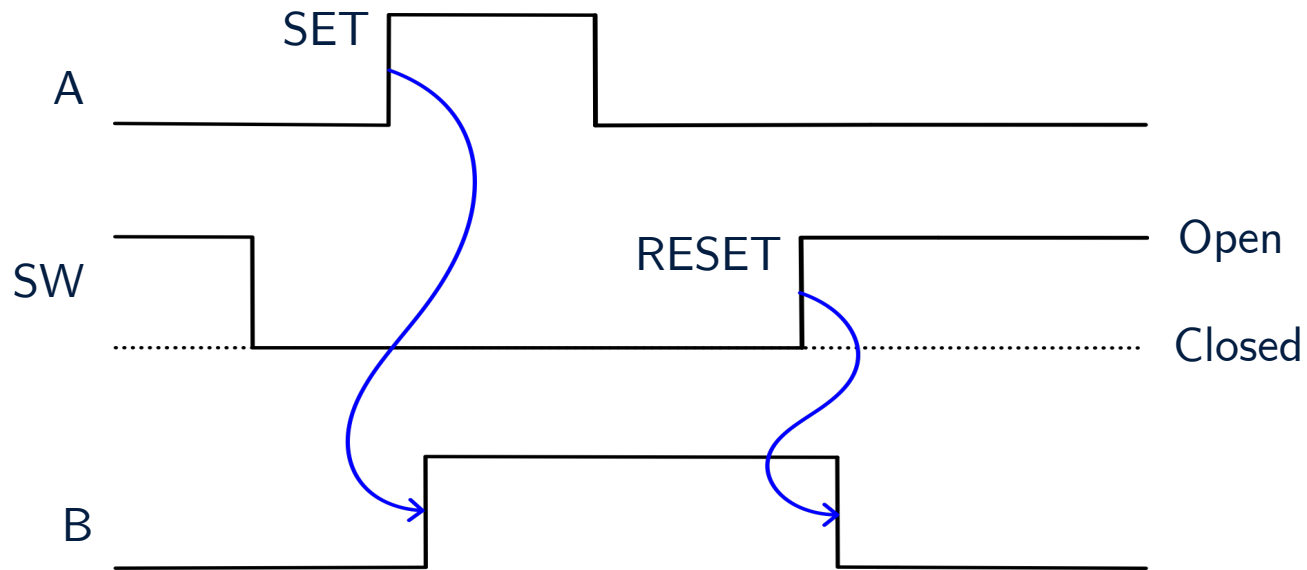
No way to reset, as after setting  $B_n = 1 \forall n$



A	B	AND
0	0	0
0	1	0
1	0	0
1	1	1
  
# Including a reset

We need a way to make the feedback signal go to 0 when we want to store a 0 bit



Next value of output was  $B_{n+1} = B_n + A$


Now reset if  $RESET = 1$ :

$$\begin{aligned}
 B_{n+1} &= B_n \cdot \overline{RESET} + A \\
 &= \overline{(\overline{B_n} + RESET)} + A \\
 \Rightarrow \overline{B_{n+1}} &= \overline{(\overline{B_n} + RESET) + A} \\
 &= \overline{(\overline{B_n} + RESET)} + SET
 \end{aligned}$$

Can implement with 2 NOR gates
 
# Including a reset

We need a way to make the feedback signal go to 0 when we want to store a 0 bit



Next value of output was  $B_{n+1} = B_n + A$


Now reset if RESET = 1:

$$B_{n+1} = B_n \cdot \overline{\text{RESET}} + A$$

$$= \overline{(\overline{B_n} + \text{RESET})} + A$$

$$\Rightarrow \overline{B_{n+1}} = \overline{(\overline{B_n} + \text{RESET})} + A$$
 
$$= \overline{(\overline{B_n} + \text{RESET})} + \text{SET}$$



Can implement with 2 NOR gates

# Overview of lectures

1. Logical functions and logic gates
2. Low level logic design
3. Binary number representation
4. Binary arithmetic
- 5. Integration of digital logic components**
6. Memory and sequential circuits
7. Design of sequential logic
8. Data converters: analogue to digital / digital to analogue

Please send feedback, comments and corrections to [mark.cannon@eng.ox.ac.uk](mailto:mark.cannon@eng.ox.ac.uk)